

# 電子電路實驗 5: Differential Amplifiers

## 實驗預報

B02901178 江誠敏

April 27, 2015

## 1 Objectives

1. To be familiar with the characteristics of differential amplifiers
2. To comprehend the importance of CMRR (Common Mode Rejection Ratio) of an amplifier.

## 2 Procedures

### 2.1 Differential Mode Small Signal Analysis

1. Use  $10\text{ k}\Omega$  variable resistance for  $R_{C1}, R_{C2}, R'$ , and  $R_{S1} = R_{S2} = 0$  in Fig. 5.
2. Provide voltage source  $V_{CC} = +12V$ , and  $V_{SS} = -6V$  to the circuit.
3. Provide voltage source  $V_{SS} = -6V$  to pin 13 of each chip of CA3046.
4. Oscilloscope ▷Press the CH1 and CH2 MENU ▷Coupling ▷AC.
5. Oscilloscope ▷Press the DISPLAY button ▷Format ▷YT mode.
6. Oscilloscope ▷Press the Measure button ▷Observe  $V_i(p-p)$  in CH1.
7. Use the function generator to provide the input small signal  $V_i$  and make sure that  $V_i = v_{ac}\sin(2\pi ft)$ ,  $2v_{ac} = 20mV(p-p)$ ,  $f = 1\sim 5kHz$  is measured from the breadboard by using CH1 of oscilloscope to observe.
8. Keep the previous adjustment of  $V_i$  constantly, and do not adjust the amplitude tuner in function generator any further.
9. Oscilloscope ▷Press the Measure button ▷Observe  $V_{O1}$  (p-p) and  $V_{O2}$  (p-p) in CH1 and CH2 at YT mode.
10. Adjust the variable resistance of  $R'$  so that voltage gain could be as high as possible.

11. Adjust the variable resistance of  $R_{C1}$  and  $R_{C2}$  so that  $A_{d1}$  voltage gain could be equal to  $A_{d2}$ .
12. If  $V_o = 0$ , that is, there is no output signal, try to generate the input small signal  $v_i$  as  $v_i = v_{ac} \sin(2\pi ft)$ ,  $2v_{ac} = 2V$  (p-p),  $f = 1 \sim 5 kHz$ , and repeat step (10) (11).
13. Record  $A_d$ :
14. Function generator ▷Press the FUNC button ▷Reducing Frequency and observe the voltage gain  $A_{V_{in}}$  oscilloscope until  $A_V = 0.707A_d$ .
15. Function generator ▷Press the FUNC button ▷Increasingly adjust the Frequency and observe the gain  $A_{V_{in}}$  oscilloscope until  $A_V = 0.707A_d$ .
16. Record the frequency
17. Change the frequency of small-signal input voltage, and record the input

## 2.2 Common Mode Small Signal Analysis

1. Keep the previous adjustment of  $R_{C1}$ ,  $R_{C2}$  and  $R'$  constantly. Use function generator to provide  $v_i = v_{ac} \sin(2\pi ft)$ ,  $2v_{ac} = 1V$  (p-p),  $f = 1 \sim 5 kHz$ .
2. Oscilloscope ▷Press the Measure button ▷Observe  $V_{O1}$  (p-p) and  $V_{O2}$  (p-p) in CH1 and CH2 at YT mode.
3. Record  $A_{cm}$
4. Function generator ▷Press the FUNC button ▷Reducing Frequency and observe the voltage gain  $A_{V_{in}}$  oscilloscope until  $A_V(\text{Low-3dB}) = 0.707A_{cm}$ .
5. Function generator ▷Press the FUNC button ▷Increasingly adjust the Frequency and observe the gain  $A_{V_{in}}$  oscilloscope until  $A_V(\text{High-3dB}) = 0.707A_{cm}$ .
6. Record the frequency.
7. Change the frequency of small-signal input voltage, and record the input and output voltage shown in oscilloscope to the following table.

## 2.3 Completed Mode Small Signal Analysis

1. Keep the previous adjustment of  $R_{C1}$ ,  $R_{C2}$  and  $R'$  constantly. Use the function generator to provide: (a)  $V_{id} = v_{ac} \sin(\omega t)$ ,  $2v_{ac} = 20mV$  (p-p), and (b)  $V_{icm} = v_{ac} \sin(2\pi ft)$ ,  $2v_{ac} = 1V$  (p-p),  $f = 1 \sim 5 kHz$ .
2. Oscilloscope ▷Press the Measure button ▷Observe  $V_{O1}$  (p-p) and  $V_{O2}$  (p-p) in CH1 and CH2 at YT mode.
3. Record  $A_d, A_{d1}, A_{d2}, A_{cm}, V_{O1}, V_{O2}$
4. Function generator ▷Press the FUNC button ▷Increasingly adjust the Frequency and observe the gain  $A_{V_{in}}$  oscilloscope until  $A_V(\text{High-3dB}) = 0.707A_{cm}$ .
5. Record the frequency.

6. Change the frequency of small-signal input voltage, and record the input and output voltage shown in oscilloscope to the following table.