

# 電子電路實驗 5: Differential Amplifiers

## 實驗結報

B02901178 江誠敏

May 11, 2015

## 1 實驗結果

### 1.1 Differential Gain

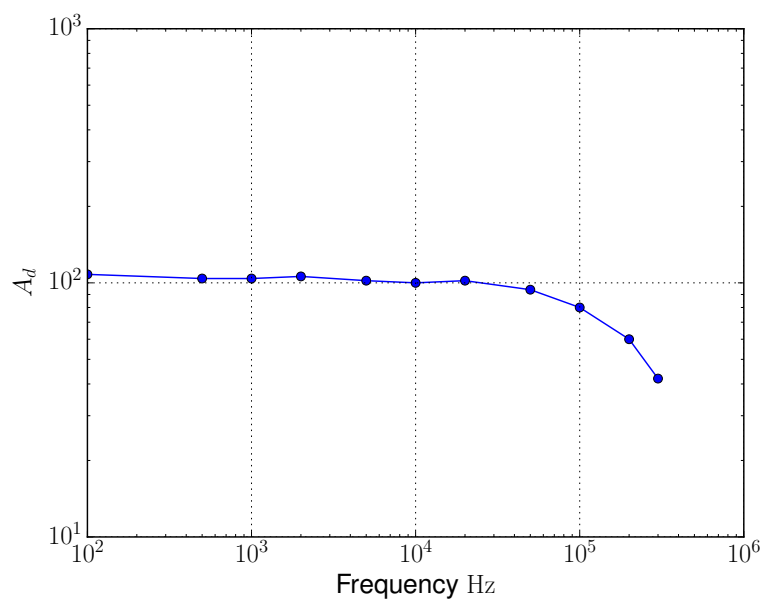


Figure 1:  $A_d$  Bode plot.

## 1.2 Common Gain

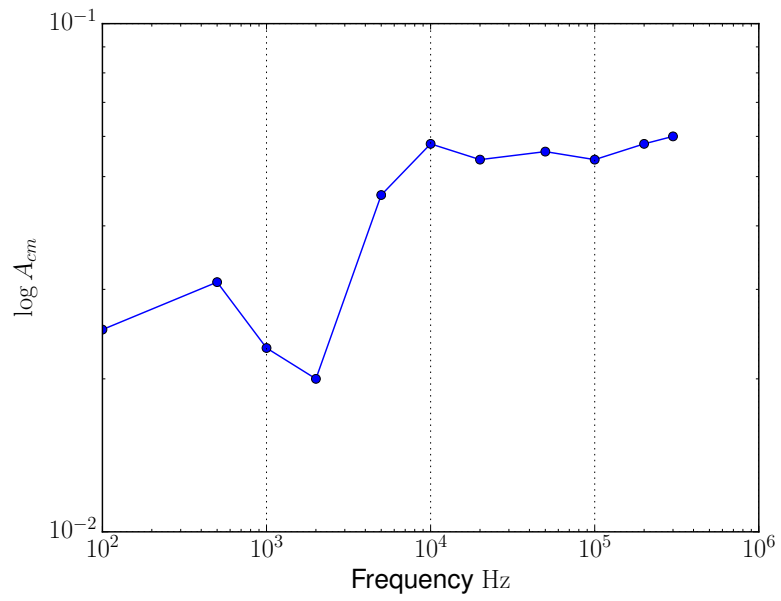


Figure 2:  $A_{cm}$  Blot plot.

## 1.3 CMRR

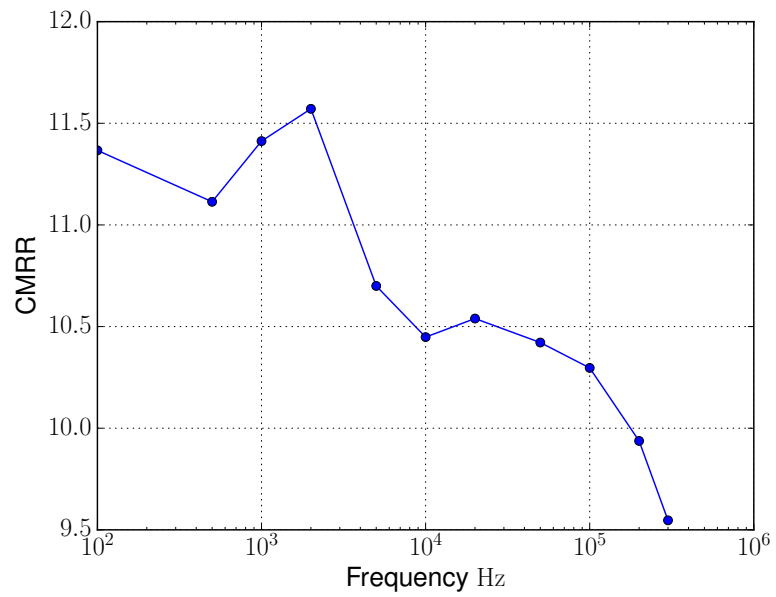


Figure 3: CMRR

## 2 結報問題

1. In Fig. 4, the differential mode input and common mode input can be adjusted independently and not be interfered for each other. Let  $I = 1\text{ mA}$ ,  $R_{C1} = R_{C2} = 10\text{ k}\Omega$ . Use PSIPCE to find:

答:

- (a) Transfer curve, where the input range of differential mode is around  $\pm 50\text{ mV}$ , and the internal resistor of the current source  $R = \infty$ .

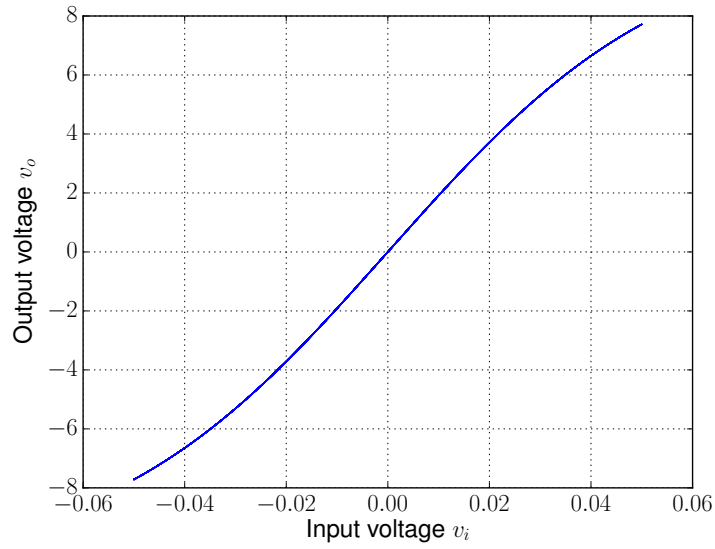


Figure 4: Transfer curve in differential mode

- (b)  $R_{id}$  and  $A_d$ , where the internal resist or of the current source  $R = \infty$ .

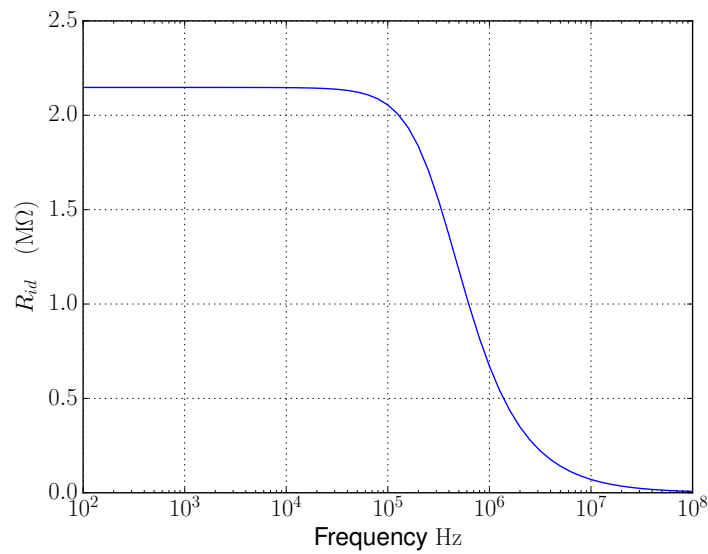


Figure 5: Plot of  $R_{id}$

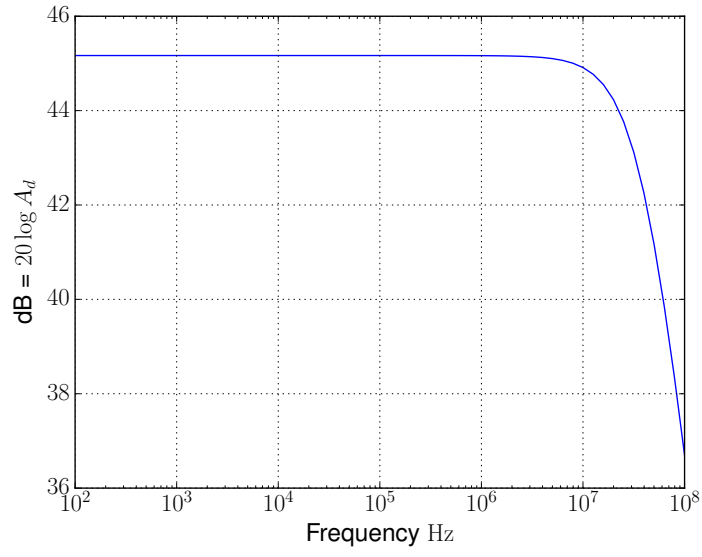


Figure 6: Bode plot of  $A_d$

(c)  $R_{icm}$  and  $A_{cm}$ , where the internal resist or of the current source  $R = \infty$ .

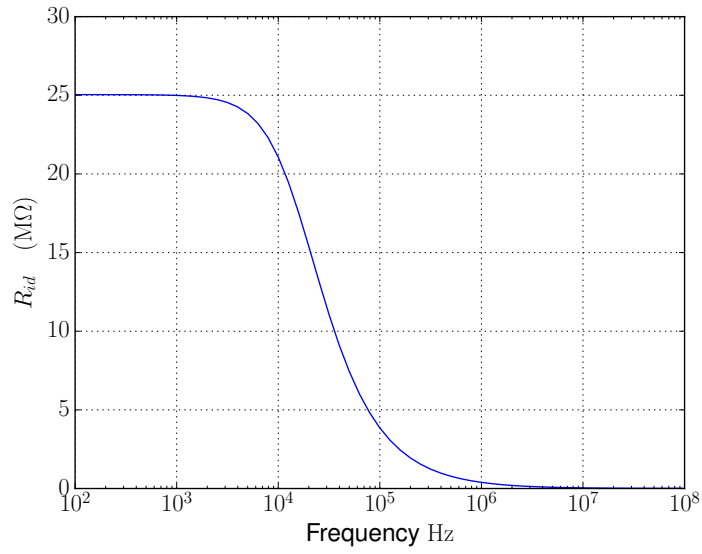


Figure 7: Plot of  $R_{icm}$

Due to the symmetry of the circuit,  $A_{cm}$  is 0.

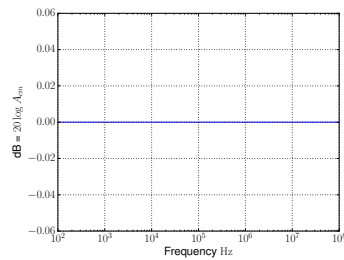


Figure 8: Bode plot of  $A_{cm}$

(d)  $R_{icm}$  and  $A_{cm}$ , where the internal resist or of the current source  $R = 200\text{ k}\Omega$ .

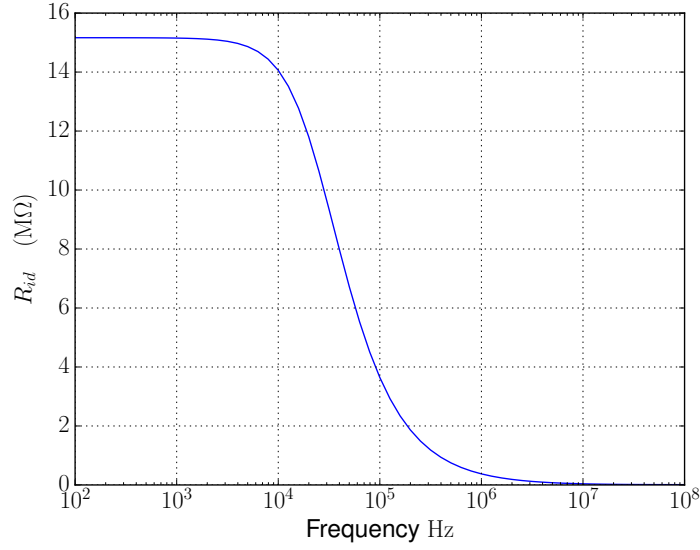


Figure 9: Plot of  $R_{icm}$

Due to the symmetry of the circuit,  $A_{cm}$  is 0.

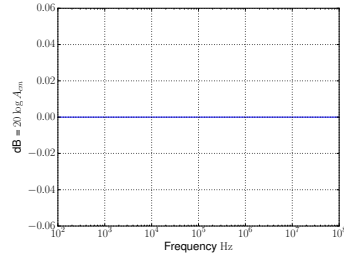


Figure 10: Bode plot of  $A_{cm}$

### 3 心得

今天自從上個月以來第一次開始做實驗。雖然過了很久記憶會模糊，不過我們都還記得一件事：出了問題，換儀器就對了！本來以為這樣就可以早早做完實驗早早去吃飯，沒想到我在檢查的時候，波形變成麥當勞波形，當場被打回票。最後弄一弄才知道原來是示波器的線鬆了。然後我們要去吃飯時店也幾乎都關了，只好去麥當勞怒吃雞塊了。