

電子電路實驗 7: Vibrator

實驗預報

B02901178 江誠敏

December 1, 2015

1 Objectives

1. To familiarize various kind of multivibrators, including bistable, monostable and unstable multivibrators.

2 Procedures

2.1 Multivibrator using the Crystal oscillator

1. Supply voltage signal $V_{CC} = 5\text{ V}$ to pin 14 of 74LS00 IC and short pin 7 to the ground.
2. Attach CH1 probe of oscilloscope in the node of the output of second NAND gate.
3. Observe whether the frequency of the measured wave is sinusoidal with frequency almost same as that of piezoelectric crystal (3.5 MHz). Record the frequency f_0 .

2.2 Circuits of Sparkling lamp

1. Supply voltage $V_{CC} = 12\text{ V}$.
2. Apply the values of $R = 220\ \Omega$, $C_1 = C_2 = 47\ \mu\text{F}$, $R_{B1} = R_{B2} = 100\ \text{k}\Omega$, $R_{C1} = R_{C2} \approx 0.5\ \text{k}\Omega$
3. Oscilloscope ▷Press the CH1 and CH2 Menu ▷Coupling ▷DC.
4. Adjust R_{B1} and R_{B2} to make the lamp be able to sparkle and make the oscillatory frequency of the lamp as ideally as you wish.
5. Record the value of oscillatory frequency f_0 .
6. Use the Cursors menu button to measure and record the value of T_H, T_L , Duty cycle , $R_{C1}, R_{C2}, R_{B1}, R_{B2}$.

2.3 An astable multivibrator using the LM555 IC

1. supply voltage $V_{CC} = 5\text{ V}$. Apply the values $R_A = R_B = 10\text{ k}\Omega$ and $C = 1$.
2. Adjust R_A, R_B to fulfill the condition of $f_0 = 100\text{ kHz}$, Duty cycle = 90% and $T_L = 1\text{ }\mu\text{s}$.
3. Attach CH1 and CH2 probes of oscilloscope to pin 3 and pin 6, respectively, and observe the measured waveform in CH1 and CH2.
4. Use the **Cursors** menu button to measure and record the value of T_L , Duty cycle .
5. Record f_0, R_A, R_B .
6. Change the supply voltage $V_{CC} = 10\text{ V}, 15\text{ V}$ and repeat the process.

2.4 The series of 555 Circuits.

2.4.1 Circuit implementation

1. Supply voltage $V_{CC} = 5\text{ V}, I_{SET} = 0.5\text{ A}$.
2. Do not connect $8\text{ }\Omega$ speaker in the following steps.
3. Use $10\text{ k}\Omega$ for R_A, R_B, R_C, R_D .
4. Attach CH1 and CH2 probes of oscilloscope to pin 3 of A_1 and $A - 2$ respectively.
5. Observe the measured wveform in CH1 and CH2.

2.4.2 Frequency Adjustment

1. Adjust R_A to have $f_1 = 300\text{ Hz} \sim 700\text{ Hz}$ and R_B to have Duty cycle = 50%.
2. Adjust R_C to have $f_2 = 0.1\text{ Hz} \sim 10\text{ Hz}$ and R_D to have Duty cycle = 50%.

2.4.3 Alarm Bell Adjustment

1. Connect $8\text{ }\Omega$ speaker.
2. Adjust R_A, R_C to have an appropriate sound.

2.4.4 Measurement

1. Record $f_1, f_2, R_A, R_B, R_C, R_D$.

2.4.5 Speaker Replacement

1. Replace the $8\text{ }\Omega$ speaker with LED, observe whether the LED twinkles.