

# 電子電路實驗 6: Linear DC Regulator

## 實驗預報

B02901178 江誠敏

May 11, 2015

## 1 Objectives

1. To familiarize with the construction and characteristics of Linear Regulator.
2. To visualize how Zener diode operate and its  $I$ - $V$  characteristics

## 2 Procedures

### 2.1 Differential Mode Small Signal Analysis

1. Use  $1\text{ k}\Omega$  resistance for  $R_2$ ,  $100\text{ k}\Omega$  variable resistance for  $R_L$ ,  $10\text{ k}\Omega$  variable resistor for  $R$ ,  $R_1$  in Fig. 2.
2. In order to measure the breakdown voltage of the Zener diode, slowly increase  $V_{DC}$  until the C.C. signal alerts in the power supply.
3. Record the  $V_{DC}$  value as breakdown voltage  $V_r$  when the C.C. signal alerts.
4. Record the breakdown voltage  $V_r$ .
5. Provide voltage source  $+15\text{ V}$ ,  $-15\text{ V}$ , and  $V_{DC} = 10\text{ V}$  to the circuit.
6. No need to use the Oscilloscope and function generator in the experiment
7. Adjust the variable resistor  $R_a$  and observe how the output voltage will change.
8. Adjust the variable resistor  $R_1$  and  $R$  until the output voltage  $V_o = 5\text{ V}$ .
9. Record the value of  $R_1, R$ . (Usually,  $R \leq 500\text{ }\Omega$ )
10. Adjust the variable resistor  $R_L$  and observe how the output voltage will change.
11. Record the output voltage  $V_o$  and  $R_L$ .
12. Keep the previous adjustment of  $R$ ,  $R_1$  constantly and adjust  $R_L = 50\text{--}100\text{ k}\Omega$ .
13. Adjust the input voltage  $V_{DC}$  and observe how the output voltage will change.
14. Record the output voltage  $V_o$  and  $V_{DC}$ .