

電子電路實驗 6: ADC/DAC

實驗預報

B02901178 江誠敏

November 23, 2015

1 Objectives

1. To study another group of analog IC circuits of great importance, data converters.

2 Procedures

2.1 Measure the voltage as full load.

1. Supply voltage signal $V_{in} = 0\text{ V}$ and V_R .
2. Slowly increase V_R from 2.50 V to 5 V . Format \triangleright YT mode.
3. Adjust V_R as the digital output just equals to 11111111.
4. Record V_R .

2.2 Measure Analog voltage value to Digital output.

1. Set $V_R = 2.5\text{ V}$ and $V_{in} = 0\text{ V}$ to 2.5 V .
2. Slowly increase V_{in} from 0 to 5 V , and record V_{in} .

2.3 DAC0800 Testing circuit

1. In Fig. 2, supply $V_{DD} = 5\text{ V}$, $V_{ref} = 5\text{ V}$ for DAC circuit and $V_{\pm} = \pm 15\text{ V}$ for $\mu\text{A}741$ OP Amp.
2. Input 11111111 to the digital input terminals.
3. Adjust $V_R = 10\text{ k}\Omega$ to have $V_{out} = 5\text{ V}$. Record the value of V_R and V_{out} .

2.4 Connection of both circuit

1. Connect DB7 to B1, DB6 to B2, ... and DB0 to B8.
2. Supply voltage $V_R = 2.5\text{ V}$ and slowly increase V_{in} from 0 to 5 V . Record V_{in} and V_{out} .